

rgpvonline.com

Roll No

EX - 304

B.E. III Semester

Examination, December 2012


Electronic Devices and Circuits - I

Time : Three Hours

Maximum Marks : 70/100

Note: Attempt any Five questions. All questions carry equal marks.

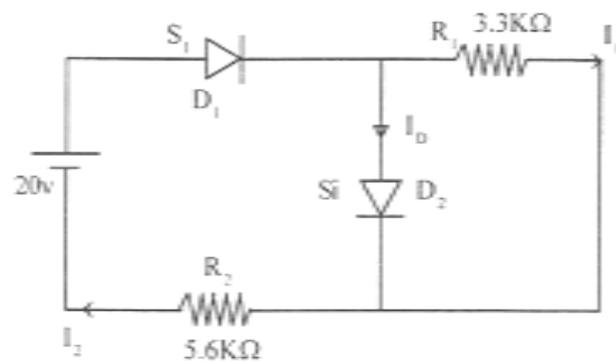
1. a) Explain the difference between Zener diode and diode.
- b) Determine the currents I_1 , I_2 and I_D for the network shown below.



2. a) Explain in brief:
 - i) Varactor diode
 - ii) Tunnel diode
 - iii) PIN diode
 - iv) LED


rgpvonline.com

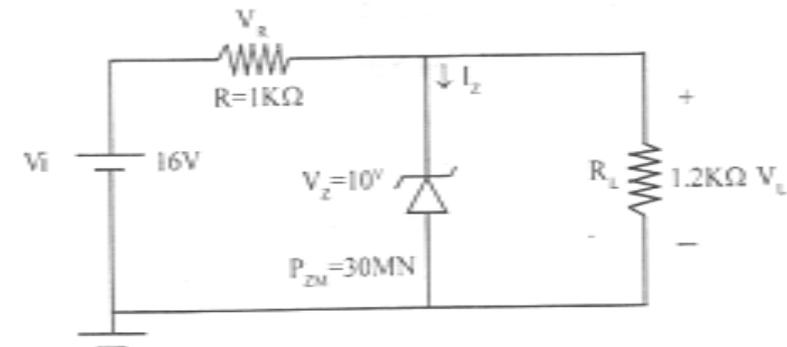- b) For the zener diode network shown below determine V_L , V_R , I_Z and P_Z .



3. a) Write the difference between an enhancement and depletion type MOSFET.
 - b) Explain the working of a JFET and give its characteristics curves.
4. a) What is the need of biasing circuit in BJT. Explain biasing techniques for BJT in brief.
 - b) Find the value of I_C , I_B and V_{CE} from the circuit given below.

rgpvonline.com

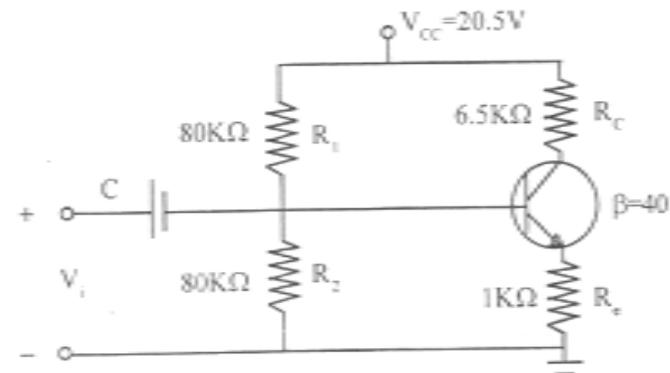

5. a) Discuss the effect of Negative feedback on gain, input impedance, output impedance, distortion, stability.
b) Draw and explain the circuit of a Wien bridge oscillator.

6. a) What do you mean by class A, class B and class C amplifiers? **rgpvonline.com**
b) Show that the maximum conversion efficiency of a Class B amplifier system is 78.5%.

7. a) Draw Bootstrapped Darlington circuit and explain how this increases the input resistance.
b) Draw and explain the circuit diagram of Darlington amplifier.

8. Short notes on (any two)
 - a) Effect of temperature on semi conductor diode.
 - b) RC coupled amplifier
 - c) V.I characteristics of VJT
 - d) Zener regulator
 - e) Clippers and clamping circuits.

rgpvonline.com