

Total No. of Questions :10]

[Total No. of Printed Pages : 2

Roll No .....

**EX - 403**

**B.E. IV Semester**

Examination, December 2012

**Digital Electronics Logic Design - I**

*Time : Three Hours*

*Maximum Marks : 70/100*

- Note:** (1) Attempt any *one* from each unit.  
(2) Assume any missing data, if any.

**UNIT - I**

1. (a) Convert the  $(250.25)_{10}$  to base 4, 8, 16.  
(b) Represent  $(8620)_{10}$  in BCD and excess 03 code.  
(c) Show 8 bit addition of the following decimal numbers in 2's complement  
45 and 56  
67 and -98

OR

2. (a) Realize following gates using minimum number of NAND gates :  
AND, OR, NOR, X-OR  
(b) Simplify the following Boolean expressions  
 $ABC + \bar{A}BC + AB\bar{C} + A\bar{B}C$   
 $BC + A\bar{C} + AB + ACD$

[2]

## UNIT - II

3. Design BCD to excess-3 code convertor circuit and draw the logic diagram.

OR

4. Design a full adder and derive the expression for output. Realize it with NAND gates.

## UNIT - III

5. What is J-K flip-flop? Explain its NAND gate implementation.

OR

6. Design the 4-bit ring counter using D-flip flops.

## UNIT - IV

7. (a) Differentiate between synchronous and asynchronous counters?  
(b) Explain a synchronous 4-bit up-down counter.

OR

8. What is shift register? How a word is stored in a serial shift register.

## UNIT - V

9. Explain the Binary weighted D/A converter.

OR

10. Write short note on any one of the following :  
(a) PAL and PLA  
(b) RAM and ROM

\*\*\*\*\*